
REQUIREMENTS NOT MET

N/A

PROBLEMS ENCOUNTERED

N/A


HOMWORK EXERCISES

HW9

6.17


a)

64x4 RAM

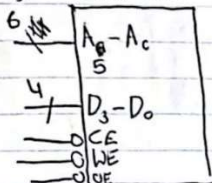


b)

4096x8 RAM

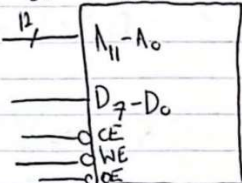

c)

64Kx8 RAM

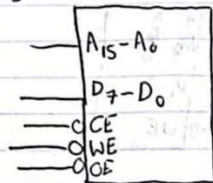

Even 6

6.18

part

Address Lines (A)	Data Lines (D)	2 ^{A+1}	Capacity (bits)
7	8	128	1024
14	4	16384	65536
10	16	1024	16384

6.19

$$A_{10}(H) \rightarrow A_{10}(L) \mid \log_2(2048) = 11$$

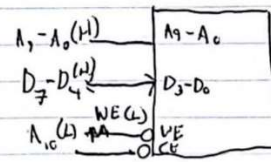
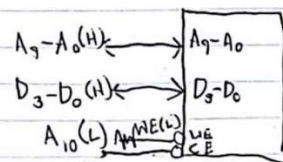
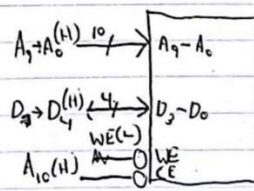
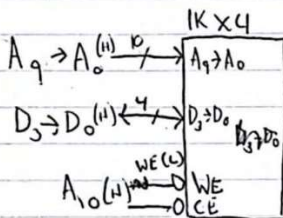


Figure 1: Homework 9 Q 6.17 - 6.19

11 10987 6543 216
0-2k: 000 0000 0000 0000 000 111 111 111
2-4k: 001 0000 0000 0000 000 111 111 111
4-6k: 010 0000 0000 0000 000 111 111 111
6-7k: 011 0000 0000 0000 000 111 111 111
7-8k: 111 0000 0000 0000 000 111 111 111

6.29) $\log_2(128) = 7$

a) Too many inputs, $8 > 7$, no

b) Yes, $6 < 7$, 8 bit output ✓

6.30)

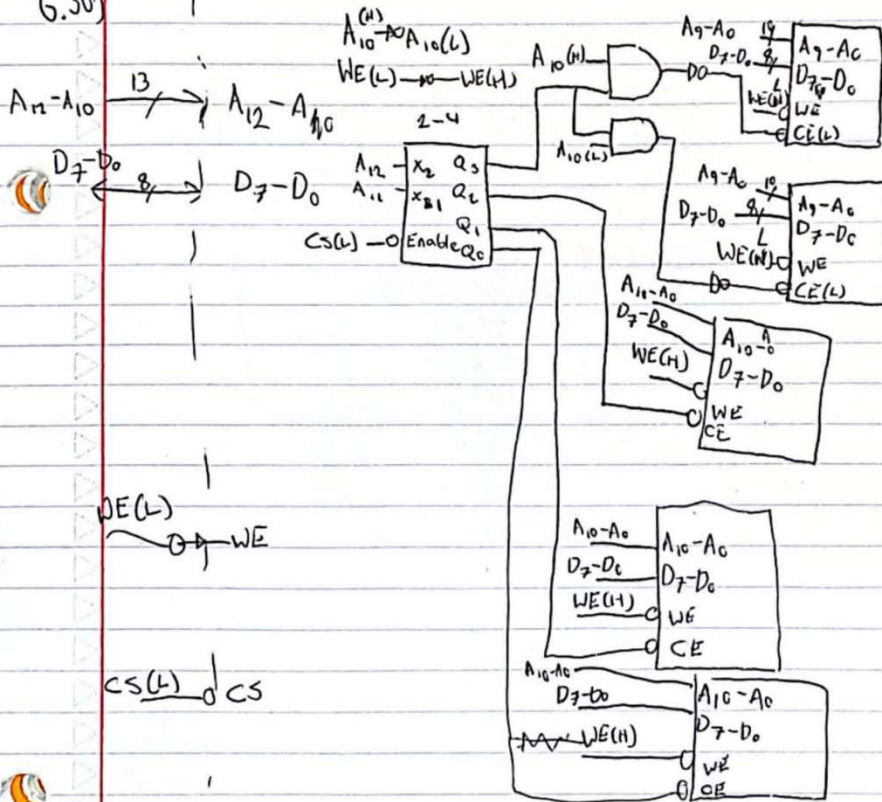


Figure 2: Homework 9 Q 6.29 & 6.30