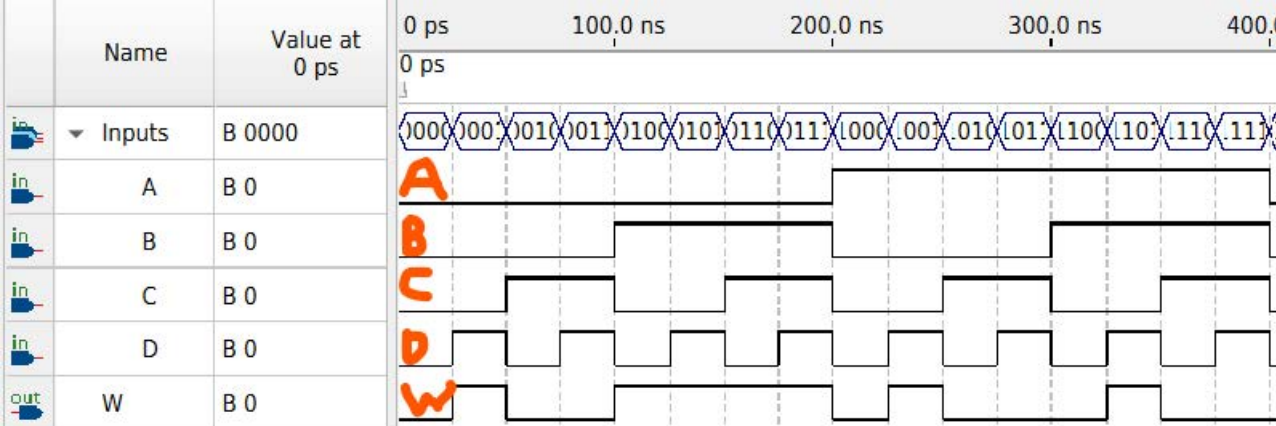




Inputs A,B,C,D count from 0000 to 1111; giving us all 16 possible input combinations. All inputs are active high, as is our output. Our output is only active at 0001, 0100-0111, 1001, and 1101.