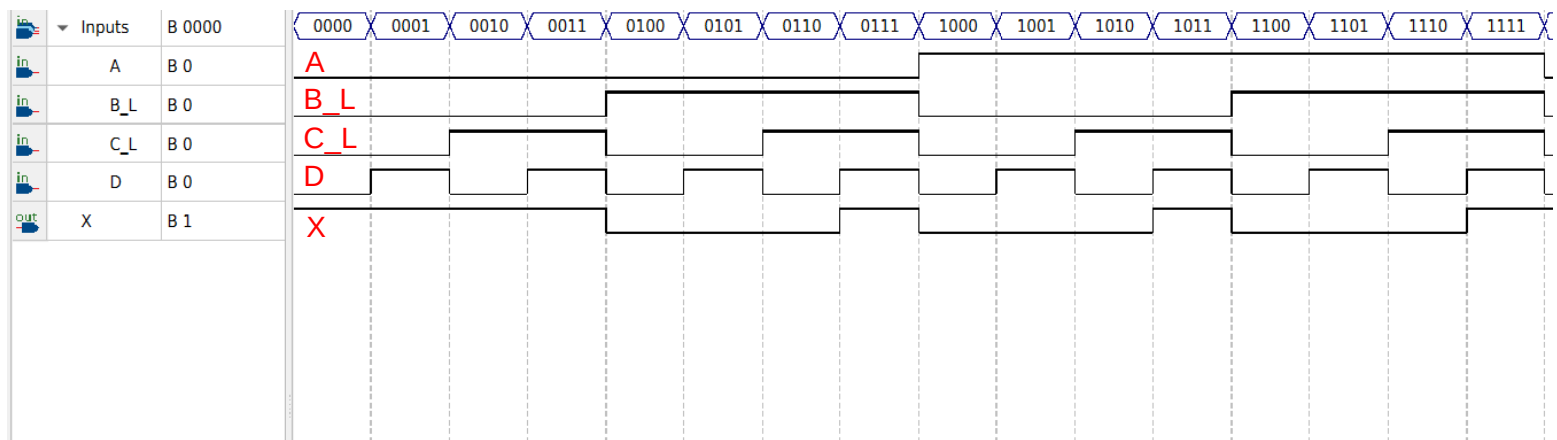




The new simulation shows a different voltage table, as a 0 for B_L and C_L became a high and a 1 for B_L and C_L became a low.

We see out values of high for 0000-0011, 0111, 1011, 1111.