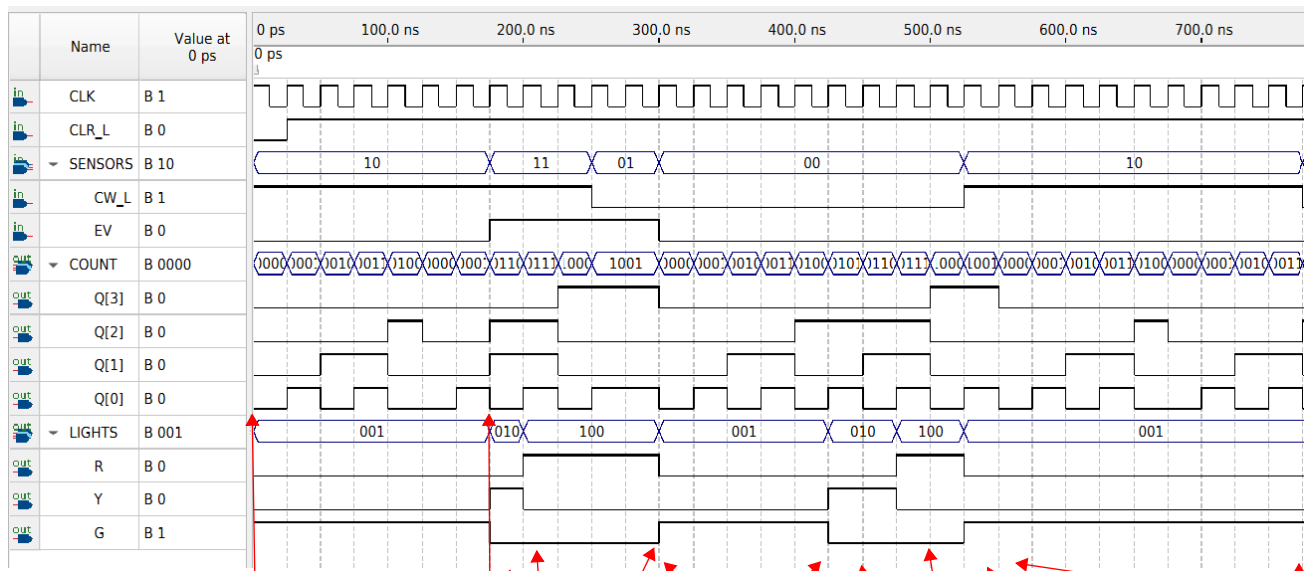




The count goes 0,1,2,3,4,0,1 as we have the EV and CW(L) signals both as false, leaving the light green.

GREEN CYCLE

The second that EV goes true, the light switches to our second bit of yellow (0110).

We then count to red (0111, 1000, 1001) and hold at 1001 until EV ends.

GREEN CYCLE

During this cycle, we will show our CW(L), we see it counts 0000-0100.

Goes to green since no EV (mealy)

We go thru red cycles, (not held since no EV).

We get two yellow cycles for CW(L): 0101, 0110.

Continues counting 0000-1000 since no EV or CW(L).